



UNIVERSITEIT•STELLENBOSCH•UNIVERSITY
jou kennisvennoot • your knowledge partner

E344 Assignment 2

Abraham Albertus Cilliers

23252162

Report submitted in partial fulfilment of the requirements of the module
Design (E) 344 for the degree Baccalaureus in Engineering in the Department of Electrical
and Electronic Engineering at Stellenbosch University.

August 21, 2021



UNIVERSITEIT • STELLENBOSCH • UNIVERSITY
jou kennisvennoot • your knowledge partner

Plagiaatverklaring / *Plagiarism Declaration*

1. Plagiaat is die oorneem en gebruik van die idees, materiaal en ander intellektuele eiendom van ander persone asof dit jou eie werk is.

Plagiarism is the use of ideas, material and other intellectual property of another's work and to present it as my own.

2. Ek erken dat die pleeg van plagiaat 'n strafbare oortreding is aangesien dit 'n vorm van diefstal is.

I agree that plagiarism is a punishable offence because it constitutes theft.

3. Ek verstaan ook dat direkte vertalings plagiaat is.


I also understand that direct translations are plagiarism.

4. Dienooreenkomstig is alle aanhalings en bydraes vanuit enige bron (ingesluit die internet) volledig verwys (erken). Ek erken dat die woordelike aanhaal van teks sonder aanhalingstekens (selfs al word die bron volledig erken) plagiaat is.

Accordingly all quotations and contributions from any source whatsoever (including the internet) have been cited fully. I understand that the reproduction of text without quotation marks (even when the source is cited) is plagiarism

5. Ek verklaar dat die werk in hierdie skryfstuk vervat, behalwe waar anders aangedui, my eie oorspronklike werk is en dat ek dit nie vantevore in die geheel of gedeeltelik ingehandig het vir bepunting in hierdie module/werkstuk of 'n ander module/werkstuk nie.

I declare that the work contained in this assignment, except where otherwise stated, is my original work and that I have not previously (in its entirety or in part) submitted it for grading in this module/assignment or another module/assignment.

23252162	
Studentenommer / <i>Student number</i>	Handtekening / <i>Signature</i>
AA. Cilliers	August 21, 2021
Voorletters en van / <i>Initials and surname</i>	Datum / <i>Date</i>

Contents

Declaration	i
List of Figures	iii
List of Tables	iv
Nomenclature	v
1. Literature	1
1.1. Charging lead acid batteries	1
1.2. Voltage regulation	1
1.3. Switching with MOSFETs	2
2. Design	3
2.1. Overview	3
2.2. High-side switch	3
2.3. Charging regulator	4
2.3.1. Voltage regulation	4
2.3.2. Current limit	4
2.3.3. Thermal analysis	4
2.4. Circuit diagram	6
3. Results	7
3.1. Simulation results	7
3.2. Measured results	8
Bibliography	9
A. GitHub Activity Heatmap	10
B. Stuff you want to include	11

List of Figures

1.1. Charge States of Lead Acid Battery [1]	1
1.2. Linear Regulator Efficiency vs V_{in}/V_o ratio [2]	2
1.3. Switch Mode On/Off Switching Voltage Square Wave [3]	2
2.1. Circuit Diagram of High-Side Switch (V_{reg} is the voltage coming from the regulator)	4
2.2. Full Circuit Diagram of Voltage Regulator and High-Side Switch	6
3.1. Output Graphs of LTSpice Simulation	7
3.2. Cursor Measurements of the Output Current through Battery and the Battery Terminal Voltage	7

List of Tables

Nomenclature

Update this list to make it applicable to your project.

Variables and functions

T_j	Junction Temperature
-------	----------------------

T_{amb}	Ambient Temperature
-----------	---------------------

Acronyms and abbreviations

Update this list to make it applicable to your project.

IC	Integrated Circuit
PV	Photovoltaic

Chapter 1

Literature

1.1. Charging lead acid batteries

Lead acid batteries are charged using the constant current constant voltage (CCCV) charge method. With this method the battery is charged as shown in figure 1.1 in 3 stages: constant current charge, topping charge and float charge. The constant current charge is where the current is kept at a constant rate and the main portion (70%) of the charging is done and the voltage rises to the peak voltage. The topping charge stage slowly decreases the current, but the voltage stays at the same level. The float charge lower the voltage to the float charge level in order to compensate for the loss caused by self-discharge. The battery is considered fully charged when the current drops below a certain set level (around 3-5% of the Ah rating), for our battery the current drawn would be around 40mA when the battery is fully charged. [1]. According to the datasheet provided by RS Pro [4] the maximum constant current rate at which our battery should be charged is 1.2A when using the constant voltage method. Our battery is fully charged at a voltage of 7.2V when the charger is still connected.

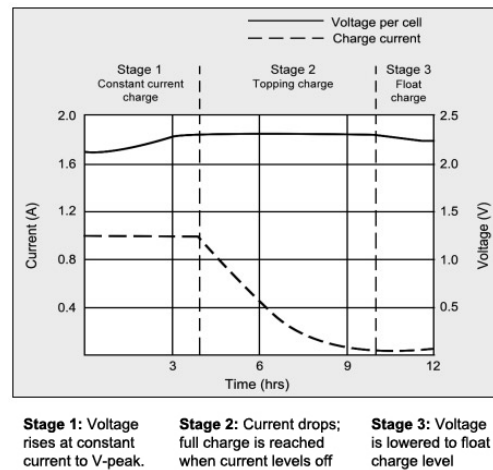


Figure 1.1: Charge States of Lead Acid Battery [1]

1.2. Voltage regulation

A voltage regulator is an integrated circuit (IC) which takes in a range of input voltages and provides a constant output voltage irrespective of a change in the load or the input voltage. Voltage regulators can be split up into two main types, linear regulators and switch-mode regulators. Linear voltage regulators work by adjusting the output voltage using a feedback

loop of resistors. It compares the output voltage to a constant reference voltage and then varies the internal resistance or current in order to keep the output voltage constant [5]. Switching regulators use an op-amp and a negative feedback loop to control a transistor. The transistor is driven so that it is either fully off or fully on, this occurs at a very high frequency and thus produces a square wave as shown in figure 1.3. The output voltage is then the average value of the square wave switching voltage [3].

Linear voltage regulators are cheap, easy to use and provide a very "clean" output voltage, however, they are not very efficient as seen in figure 1.2 they are limited in efficiency by the ratio of V_{in}/V_{out} . They also dissipate excess power in the form of heat and thus very often require the use of heat sinks to keep them cool. Switch-mode regulators are much more efficient because they store excess power, however they are more expensive and are much more complicated to design and work with.

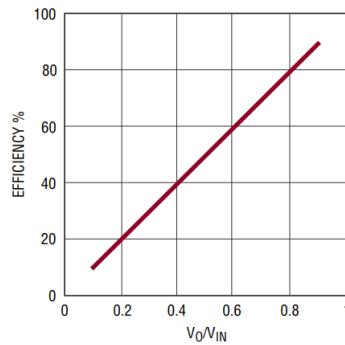


Figure 1.2: Linear Regulator Efficiency vs V_{in}/V_o ratio [2]

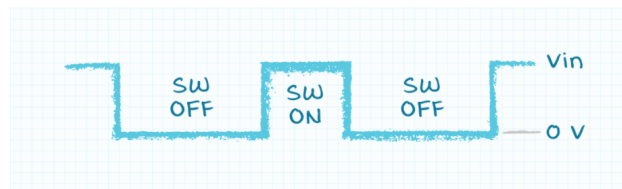


Figure 1.3: Switch Mode On/Off Switching Voltage Square Wave [3]

1.3. Switching with MOSFETs

Metal Oxide Semiconductor Field Effect Transistors (MOSFET) are a voltage controlled field effect transistor. The gate terminal is isolated from the main current carrying channel between the drain and source, as no current flows into the gate terminal [6]. Enhancement type MOSFETs requires a voltage across the gate-source terminals in order to switch the device on. Thus, the enhancement mode MOSFET acts as a normally open switch. In an NMOS (n-channel) MOSFET the device will only switch on and allow current to flow when $V_{gs} > V_{TH}$. For a PMOS (p-channel) MOSFET the opposite is true, a negative gate-source voltage will turn the transistor on, or in other words $V_{sg} > V_{TH}$.

Chapter 2

Design

2.1. Overview

The charging circuit consists of two main parts, the high-side switch and the voltage regulator. As shown in [figure xxx](#) the voltage regulator will receive its input from either an AC/DC power adapter or from a solar PV module. The voltage regulator will take an input and regulate it down to around 7.4-7.8V. The output from the voltage regulator will be used as the input to the high-side switch which is used to turn the charging circuit on/off. This design will ensure that the output voltage at the battery terminals is 7.2V after all the voltage drops have been taken into account. [reason for reg on the left of switch & block diagram](#)

2.2. High-side switch

In order to design a high-side switch that uses logic level voltages (0-5V or 0-3.3V) we need to make use of a complementary pair of PMOS and NMOS MOSFETs. Pullup resistor R3 is added to keep the p-channel MOSFET off in unknown floating voltage states. Similarly a pulldown resistor R4 is added to the gate of the n-channel MOSFET to keep it off in unknown states. Resistor R3 in figure 2.1 is also used to limit the amount of current that flows through the n-channel MOSFET. If the control voltage LoadOn is at a high of 5V the n-channel MOSFET will be turned on, thus pulling the gate of the p-channel MOSFET to ground and turning it on. According to the 2N7000 n-channel MOSFET datasheet the maximum current that can flow through the drain-source channel is 200mA, thus the minimum resistor value for R3 can be calculated as:

$$R3_{min} = \frac{7.8V}{200mA}$$
$$R3_{min} = 39\Omega$$

This value was designed for extremities and would most likely not work in the physical circuit as it is a very small resistor and it is the minimum resistance value that R3 can be, I chose a value of $100k\Omega$ as a design choice.

What I expect to happen is that when the LoadOn voltage is at a low the n-channel MOSFET will be off as the turn-on condition will not have been met and thus the p-channel

MOSFET will also be off. When the LoadOn voltage LoadOn is at a high of 5V the n-channel MOSFET will be turned on, thus pulling the gate of the p-channel MOSFET to ground and turning it on. This will allow current to flow through the drain-source channel of the p-channel MOSFET. Calculating the expected voltage at $V_{battery}$ by using a KVL loop: $-V_{regulator} - V_{DS} + V_{diode} + V_{battery} = 0$ we get an expected value of 7.2V for $V_{battery}$.

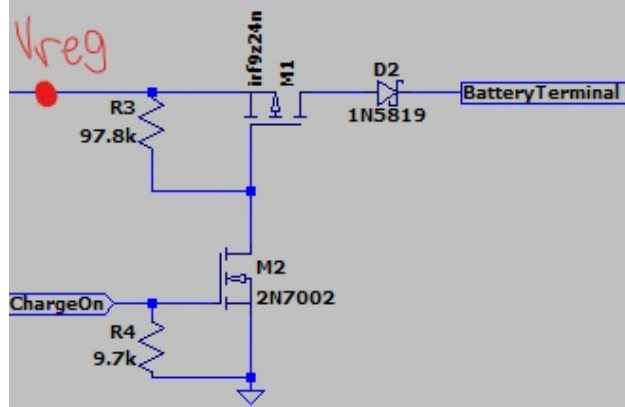


Figure 2.1: Circuit Diagram of High-Side Switch (V_{reg} is the voltage coming from the regulator)

2.3. Charging regulator

2.3.1. Voltage regulation

must still do

Show the design calculations, including resistor values, and justify design choices. Detail the range of valid input voltages for your designed regulator circuit.

2.3.2. Current limit

must still do

Explain why the charging circuit requires a maximum current limit, and how your choice of current limit was arrived at and implemented. Explain the limitations of this implementation.

2.3.3. Thermal analysis

According to the LM317 datasheet [7] the maximum junction temperature is $T_j = 125^\circ\text{C}$. This means that without a heatsink on an average day at an ambient temperature of 25°C Celsius and using the 12 DC power supply the maximum power that the regulator can dissipate is:

$$P_{max} = \frac{(T_j - T_{amb})}{\theta_{j-a}} \quad \text{with } \theta_{j-a} = 50^\circ\text{C/W}$$

$$P_{max} = 2W$$

When adding a small TO-220 package heatsink the maximum power dissipated becomes:

$$\theta_{j-c} = 5^{\circ}C/W$$

$$\theta_{c-s} = 1.64^{\circ}C/W$$

$$\theta_{s-a} = 24.4^{\circ}C/W$$

$$P_{max} = \frac{(T_j - T_{amb})}{\theta_{j-c} + \theta_{c-s} + \theta_{s-a}}$$

$$P_{max} = 3.22W$$

Thus we can see that adding a heatsink we can dissipate an extra 1.22W of power.

Without a heatsink:

Using the 12V DC supply:

$$P_{dissipated} = (V_{in} - V_{out})I_{out}$$

$$P_{dissipated} = 1.68W$$

$$\therefore T_j = P_{dissipated}(\theta_{j-a} + T_{amb})$$

$$T_j = 109^{\circ}C$$

Using the Solar PV Module (21.6V):

$$P_{dissipated} = (V_{in} - V_{out})I_{out}$$

$$P_{dissipated} = 5.52W$$

$$\therefore T_j = P_{dissipated}(\theta_{j-a}) + T_{amb}$$

$$T_j = 301^{\circ}C$$

With a heatsink:

Using the 12V DC supply:

$$P_{dissipated} = (V_{in} - V_{out})I_{out}$$

$$P_{dissipated} = 1.68W$$

$$\therefore T_j = P_{dissipated}(\theta_{j-c} + \theta_{c-s} + \theta_{s-a}) + T_{amb}$$

$$T_j = 77.14^{\circ}C$$

Using the Solar PV Module (21.6V):

$$P_{dissipated} = (V_{in} - V_{out})I_{out}$$

$$P_{dissipated} = 5.52W$$

$$\therefore T_j = P_{dissipated}(\theta_{j-a}) + T_{amb}$$

$$T_j = 196.34^{\circ}C$$

Thus we can see that adding a heatsink greatly improves the performance of the voltage regulator and keeps the junction temperature cool when using the 12 DC supply. However if we were to use the solar PV module the voltage regulator would still burn out, so we would need to implement some overvoltage protection in order to limit the amount of voltage the solar PV module can provide.

2.4. Circuit diagram

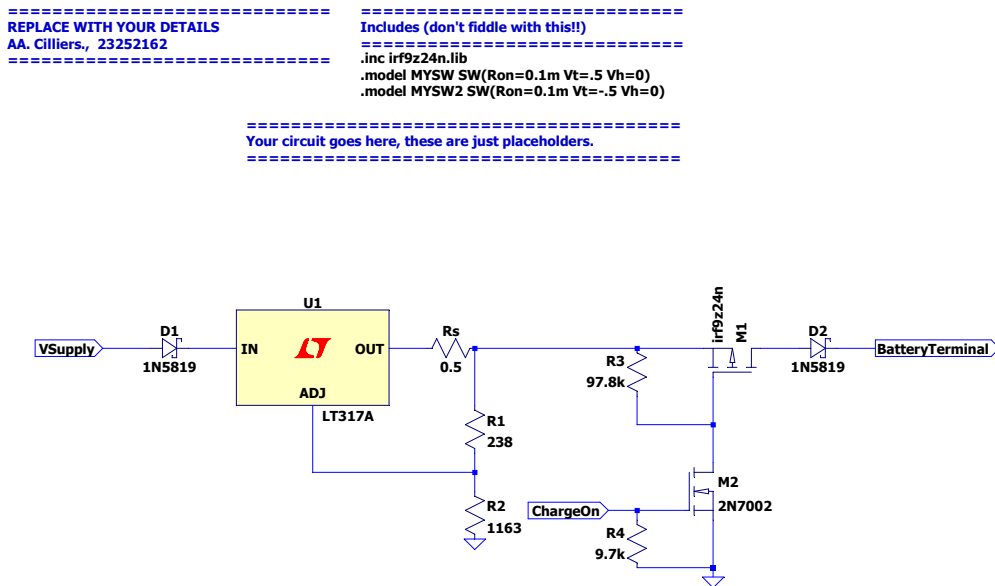


Figure 2.2: Full Circuit Diagram of Voltage Regulator and High-Side Switch

Chapter 3

Results

3.1. Simulation results

Figure 3.1 shows the output of the simulated circuit where $V(\text{batteryterminal})$ is the voltage at the battery terminals and $I(\text{Rsensebattery})$ is the output current through the battery terminal. The charging circuit only switches on when the 5V logic control signal (V_{chargeon}) is set high and the battery does not discharge when V_{supply} is switched off. The current requirement of less than 400mA when the battery is flat (at 6V) is fulfilled since the circuit only pulls 326.82mA . The final voltage when the battery is fully charged is 7.28V , thus also meeting the required design specification of 7.2V (with a 5% tolerance). Thus this design is working as intended and meets all the requirements during the simulation.

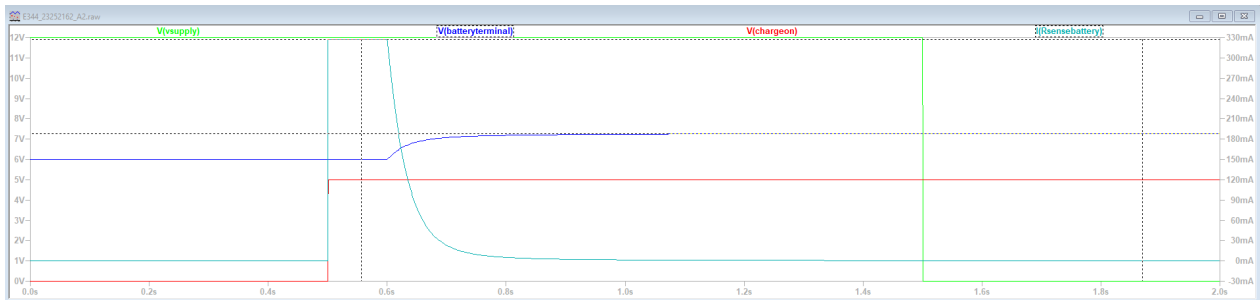


Figure 3.1: Output Graphs of LTSpice Simulation

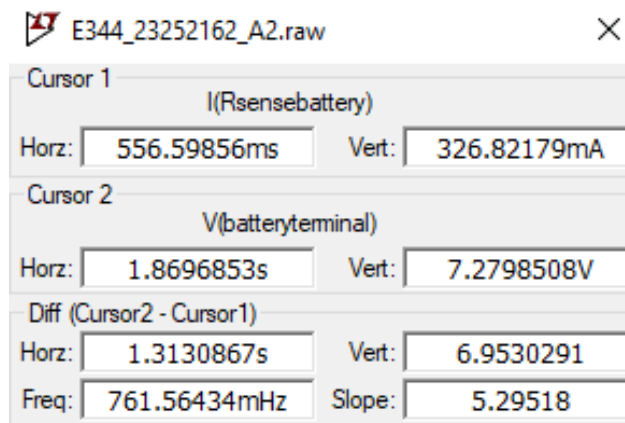


Figure 3.2: Cursor Measurements of the Output Current through Battery and the Battery Terminal Voltage

3.2. Measured results

Convince the reader that your circuit performed as expected using measured results. Same principle as for the simulation results, but now with measurements (e.g. oscilloscope plots).


Bibliography

- [1] B. University, “Bu-403: Charging lead acid,” <https://batteryuniversity.com/article/bu-403-charging-lead-acid>, Nov. 2019.
- [2] H. Zhang, “Basic concepts of linear regulator and switching mode power supplies,” <https://www.analog.com/en/app-notes/an-140.html>.
- [3] C. Incorporated, “A comparison between dc switching regulators and linear regulators,” <https://www.cui.com/blog/a-comparison-between-dc-switching-regulators-and-linear-regulators>, Dec. 2020.
- [4] *Sealed Lead-Acid Battery General Purpose Specification*, Sealed Lead-Acid Battery 537-5422(6V4.0Ah) datasheet, RS Pro.
- [5] J. Electronics, “Electronics fundamentals: Voltage regulator,” <https://www.jameco.com/Jameco/workshop/learning-center/voltage-regulator.html>, Apr. 2011.
- [6] E. Tutorials, “The mosfet,” https://www.electronics-tutorials.ws/transistor/tran_6.html, Jul. 2021.
- [7] *1.2 V to 37 V adjustable voltage regulators*, LM317 Datasheet, STMicroelectronics.

Appendix A

GitHub Activity Heatmap

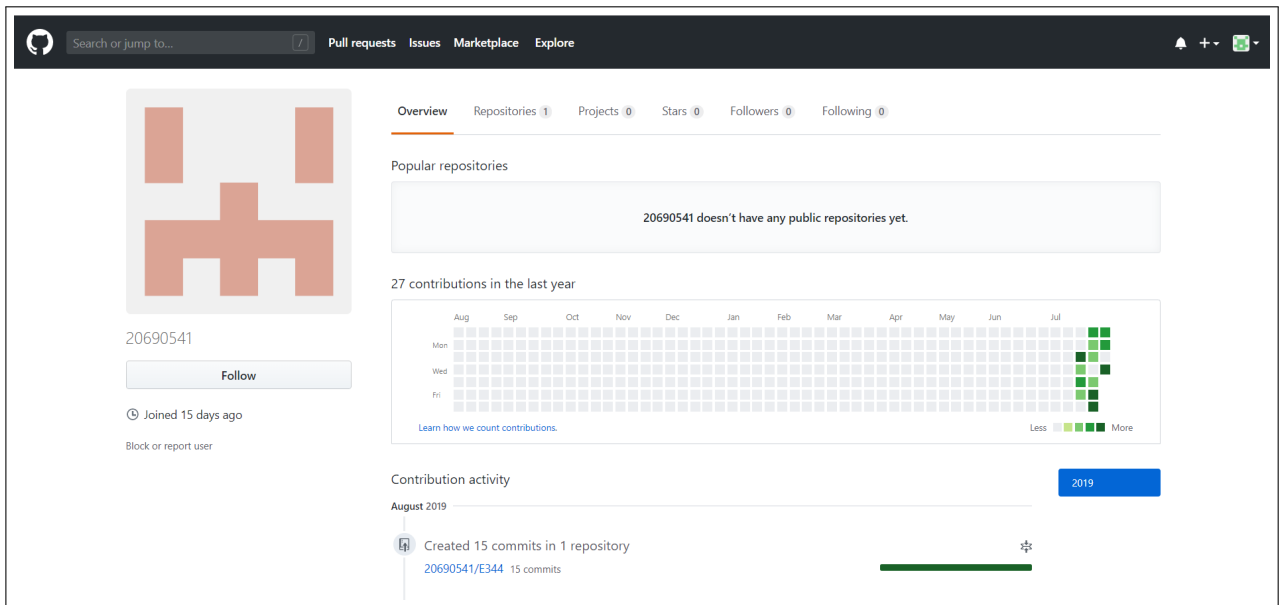Take a screenshot of your github version control activity heatmap and insert here.



Appendix B

Stuff you want to include

remove this!!

Lorem ipsum dolor sit amet, consectetur adipiscing elit. Ut purus elit, vestibulum ut, placerat ac, adipiscing vitae, felis. Curabitur dictum gravida mauris. Nam arcu libero, nonummy eget, consectetur id, vulputate a, magna. Donec vehicula augue eu neque. Pellentesque habitant morbi tristique senectus et netus et malesuada fames ac turpis egestas. Mauris ut leo. Cras viverra metus rhoncus sem. Nulla et lectus vestibulum urna fringilla ultrices. Phasellus eu tellus sit amet tortor gravida placerat. Integer sapien est, iaculis in, pretium quis, viverra ac, nunc. Praesent eget sem vel leo ultrices bibendum. Aenean faucibus. Morbi dolor nulla, malesuada eu, pulvinar at, mollis ac, nulla. Curabitur auctor semper nulla. Donec varius orci eget risus. Duis nibh mi, congue eu, accumsan eleifend, sagittis quis, diam. Duis eget orci sit amet orci dignissim rutrum.

Nam dui ligula, fringilla a, euismod sodales, sollicitudin vel, wisi. Morbi auctor lorem non justo. Nam lacus libero, pretium at, lobortis vitae, ultricies et, tellus. Donec aliquet, tortor sed accumsan bibendum, erat ligula aliquet magna, vitae ornare odio metus a mi. Morbi ac orci et nisl hendrerit mollis. Suspendisse ut massa. Cras nec ante. Pellentesque a nulla. Cum sociis natoque penatibus et magnis dis parturient montes, nascetur ridiculus mus. Aliquam tincidunt urna. Nulla ullamcorper vestibulum turpis. Pellentesque cursus luctus mauris.

Nulla malesuada porttitor diam. Donec felis erat, congue non, volutpat at, tincidunt tristique, libero. Vivamus viverra fermentum felis. Donec nonummy pellentesque ante. Phasellus adipiscing semper elit. Proin fermentum massa ac quam. Sed diam turpis, molestie vitae, placerat a, molestie nec, leo. Maecenas lacinia. Nam ipsum ligula, eleifend at, accumsan nec, suscipit a, ipsum. Morbi blandit ligula feugiat magna. Nunc eleifend consequat lorem. Sed lacinia nulla vitae enim. Pellentesque tincidunt purus vel magna. Integer non enim. Praesent euismod nunc eu purus. Donec bibendum quam in tellus. Nullam cursus pulvinar lectus. Donec et mi. Nam vulputate metus eu enim. Vestibulum pellentesque felis eu massa.

Quisque ullamcorper placerat ipsum. Cras nibh. Morbi vel justo vitae lacus tincidunt ultrices. Lorem ipsum dolor sit amet, consectetur adipiscing elit. In hac habitasse platea dictumst. Integer tempus convallis augue. Etiam facilisis. Nunc elementum fermentum wisi. Aenean placerat. Ut imperdiet, enim sed gravida sollicitudin, felis odio placerat quam, ac pulvinar elit purus eget enim. Nunc vitae tortor. Proin tempus nibh sit amet nisl. Vivamus quis tortor vitae risus porta vehicula.

Fusce mauris. Vestibulum luctus nibh at lectus. Sed bibendum, nulla a faucibus semper, leo velit ultricies tellus, ac venenatis arcu wisi vel nisl. Vestibulum diam. Aliquam pellentesque,

augue quis sagittis posuere, turpis lacus congrue quam, in hendrerit risus eros eget felis. Maecenas eget erat in sapien mattis porttitor. Vestibulum porttitor. Nulla facilis. Sed a turpis eu lacus commodo facilis. Morbi fringilla, wisi in dignissim interdum, justo lectus sagittis dui, et vehicula libero dui cursus dui. Mauris tempor ligula sed lacus. Duis cursus enim ut augue. Cras ac magna. Cras nulla. Nulla egestas. Curabitur a leo. Quisque egestas wisi eget nunc. Nam feugiat lacus vel est. Curabitur consectetur.

Suspendisse vel felis. Ut lorem lorem, interdum eu, tincidunt sit amet, laoreet vitae, arcu. Aenean faucibus pede eu ante. Praesent enim elit, rutrum at, molestie non, nonummy vel, nisl. Ut lectus eros, malesuada sit amet, fermentum eu, sodales cursus, magna. Donec eu purus. Quisque vehicula, urna sed ultricies auctor, pede lorem egestas dui, et convallis elit erat sed nulla. Donec luctus. Curabitur et nunc. Aliquam dolor odio, commodo pretium, ultricies non, pharetra in, velit. Integer arcu est, nonummy in, fermentum faucibus, egestas vel, odio.

Sed commodo posuere pede. Mauris ut est. Ut quis purus. Sed ac odio. Sed vehicula hendrerit sem. Duis non odio. Morbi ut dui. Sed accumsan risus eget odio. In hac habitasse platea dictumst. Pellentesque non elit. Fusce sed justo eu urna porta tincidunt. Mauris felis odio, sollicitudin sed, volutpat a, ornare ac, erat. Morbi quis dolor. Donec pellentesque, erat ac sagittis semper, nunc dui lobortis purus, quis congrue purus metus ultricies tellus. Proin et quam. Class aptent taciti sociosqu ad litora torquent per conubia nostra, per inceptos hymenaeos. Praesent sapien turpis, fermentum vel, eleifend faucibus, vehicula eu, lacus.